

## Task 1

### Task 1.a

The signal is given by  $V = V_m \cos(\omega t)$  as shown in the figure. Find  $V_m$  and  $\omega$ .

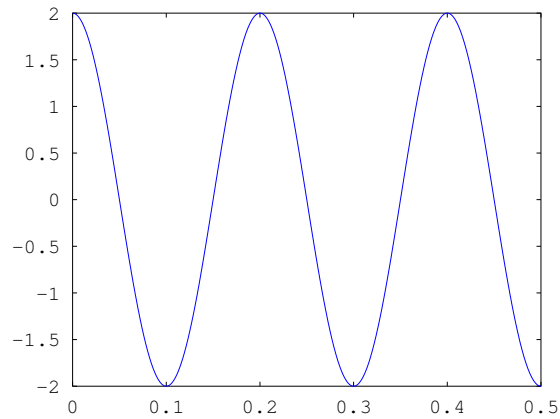


Figure 1:  $V = V_m \cos(\omega t)$

### Task 1.b

Find the period  $T$  and the frequency  $f = \frac{1}{T}$ . Show that  $\omega = 2\pi f$ .

### Task 1.c

What is the amplitude, and what is the peak-to-peak value?

### Task 1.d

The signal is changed to

$$V = V_m \cos(\omega t + \phi)$$

where  $\phi$  is the phase angle. Find the phase angle from the figure

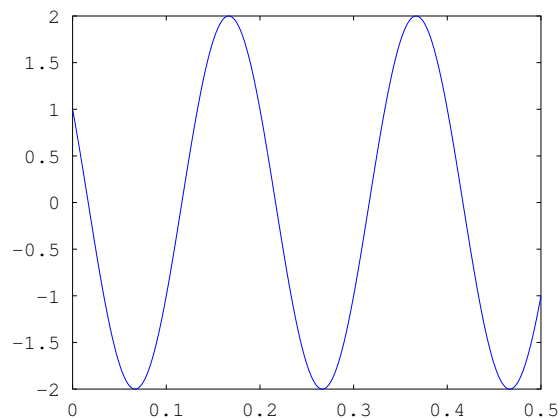


Figure 2:  $V = V_m \cos(\omega t + \phi)$

## Task 1 Solution

### Task 1.a Solution

By looking at the figure, it can be seen that the amplitude of the function is 2, since the function oscillates between 2 and -2. Therefore  $V_m = 2$

By looking at the graph we notice that the cosine function performs 5 cycles in 1 s. This means that  $\omega t$  goes from 0 to  $5 \cdot 2\pi$  when  $t$  goes from 0 s to 1 s, hence  $\omega = 10\pi$ .

### Task 1.b Solution

The period is found again from the figure, and is 0.2. The frequency is  $f = \frac{1}{T} = \frac{1}{0.2} = 5$ . We then find that  $2\pi f = 10\pi$  which is the same as  $\omega$  from the previous task.

### Task 1.c Solution

The amplitude is the same as  $V_m$  and is therefore 2. Peak-to-peak value is the difference between the top and bottom value. This is also given as two times the amplitude, in this case 4.

### Task 1.d Solution

By looking at the figure, it can be seen that the function crosses the y-axis at 1 when x is 0. This means that  $2 \cos(\phi) = 1$  which leads to  $\phi = \arccos(\frac{1}{2}) = \frac{\pi}{3} \approx 1.0472$

## Task 2

The AC current is given by the phasor

$$I = I_0 \exp j\omega t$$

where  $I_0 = 1 \text{ mA}$  and the period is  $T = 0.01 \text{ s}$ . It is given that  $\omega T = 2\pi$ .

### Task 2.a

What is the real current corresponding to the phasor  $I$ ?

### Task 2.b

The current runs through an impedance

$$Z = \frac{1}{j\omega C}, \text{ where } C = 1 \mu\text{F}$$

which is depicted in Figure 3. What is the voltage phasor  $V$ ?

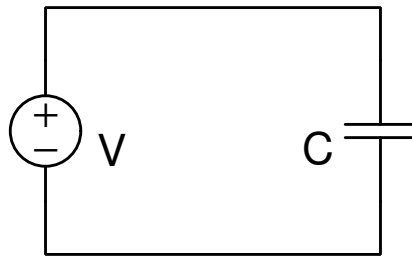


Figure 3: Capacitor circuit

### Task 2.c

What is the real voltage?

### Task 2.d

A resistor  $R = 2\text{ k}\Omega$  is inserted in series with the capacitor, which is depicted in Figure 4. The current is still  $I = I_0 e^{j\omega t}$ . What is the impedance of the two circuit elements combined?

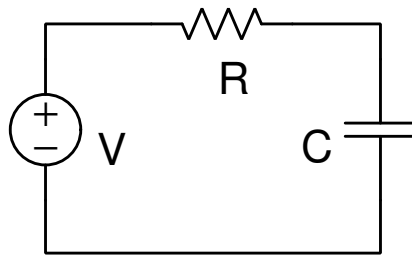


Figure 4: RC circuit

### Task 2.e

What is the resulting voltage phasor?

## Task 2 Solution

### Task 2.a Solution

The real current is defined as  $\text{Re}[I]$ . By using Euler's formula  $e^{jax} = \cos(ax) + j \sin(ax)$  we see that  $I$  can be written as  $I = I_0 e^{j\omega t} = I_0 (\cos(\omega t) + j \sin(\omega t))$ . The real value is therefore  $\text{Re}[I] = I_0 \cos(\omega t) = \cos(200\pi t)\text{mA}$

### Task 2.b Solution

We have that  $I_0 e^{j\omega t}$  and  $Z = \frac{1}{j\omega C}$  which we use to calculate the voltage

$$V = IZ = I_0 \exp(j\omega t) \frac{1}{j\omega C} = \frac{1 \text{ mA}}{1 \mu\text{F} \cdot \omega} \frac{\exp(j\omega t)}{j} = \frac{5}{\pi} \exp(j200\pi t - j\frac{\pi}{2})\text{V}$$

### Task 2.c Solution

By Eulers formula we find the real part of the voltage phasor

$$V_{Re} = \text{Re}[V] = \frac{5}{\pi} \cos(200\pi t - \frac{\pi}{2})V$$

### Task 2.d Solution

$$Z_{TOT} = Z_R + Z_C = R + \frac{1}{j\omega C} = R - \frac{j}{\omega C} = 2 \text{ k}\Omega - j \frac{1}{\pi 200 \text{ s}^{-1} \times 1 \mu\text{F}} = \left(2000 - j \frac{5000}{\pi}\right) \Omega$$

### Task 2.e Solution

$$\begin{aligned} V &= ZI = I_0 \exp(j\omega t) \left(R - j \frac{1}{\omega C}\right) \\ Z &= R - j \frac{1}{\omega C} = R - \frac{1}{\omega C} \exp\left(\frac{j\pi}{2}\right) \\ V &= R \exp(j\omega t) - \frac{1}{\omega C} \exp\left(j\left(\omega t + \frac{\pi}{2}\right)\right) \\ &= 2 \exp(j200\pi t) - \frac{5}{\pi} \exp\left(j200\pi t + j \frac{\pi}{2}\right)V \end{aligned}$$

## Task 3

Given the parts in Figure 5 (PINX, 5V and GND are pins on a microcontroller) and the code in Code 1, make the LED blink.

Code 1: Blink code for microcontroller

```
void setup(){
  pinMode(11, OUTPUT);
}

void loop(){
  digitalWrite(11, HIGH);
  delay(1000);
  digitalWrite(11, LOW);
  delay(1000);
}
```

## Task 3 Solution

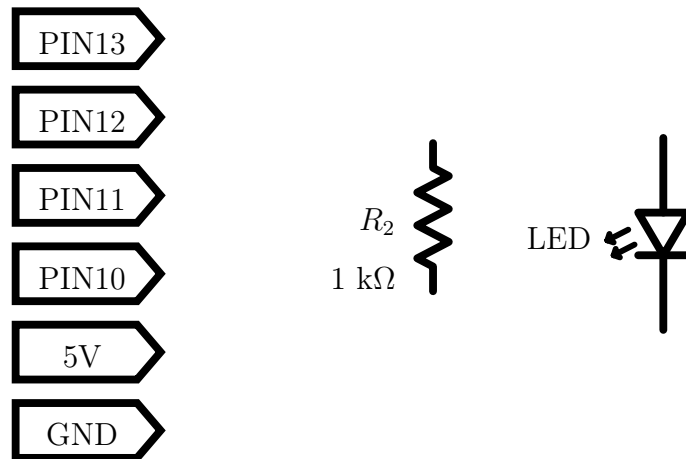


Figure 5: Components for circuit

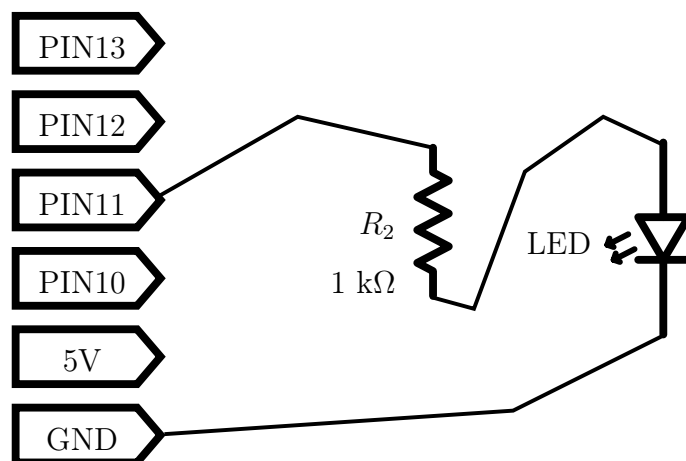


Figure 6: Solution for task 3