

Task 1

Task 1.a

4 bytes are given by the hex digits 3A F0 00 00.

What is the corresponding digits for the 4 bytes?

Task 1.b

A variable is stored in 4 bytes with 32 bits in total. The bits are numbered from 0 to 31 and are b_0, b_1, \dots, b_{31}

The variable is declared as a float with numerical value

$$a = (-1)^{b_{31}} \left(1 + \sum_{i=1}^{23} b_{23-i} 2^{-i} \right) \cdot 2^{\text{exponent}-127}$$

where *exponent* is an unsigned integer in the range 0-255 stored in the 8 bits $b_{23}, b_{24}, \dots, b_{30}$

What is a when the 4 bytes are given by the hex numbers 3A F0 00 00?

Task 1 Solution

Task 1.a

The corresponding digits are 00111010111100000000000000000000.

Task 1.b

By using the formula: $a = 0.0018310547$.

Task 2

Task 2.a

What is the function of the circuit? Explain how it works.

Task 2 Solution

Task 2.a Solution

This is a 4 bit data register, where bits b_0, b_1, b_2, b_3 is stored in D-latch 1, 2, 3 og 4.

The D-latch functions so that Q_x will not change if Load is low. If load is high, Q_x will follow D_x . When Read is high, you can read the values of the bits in R_x .

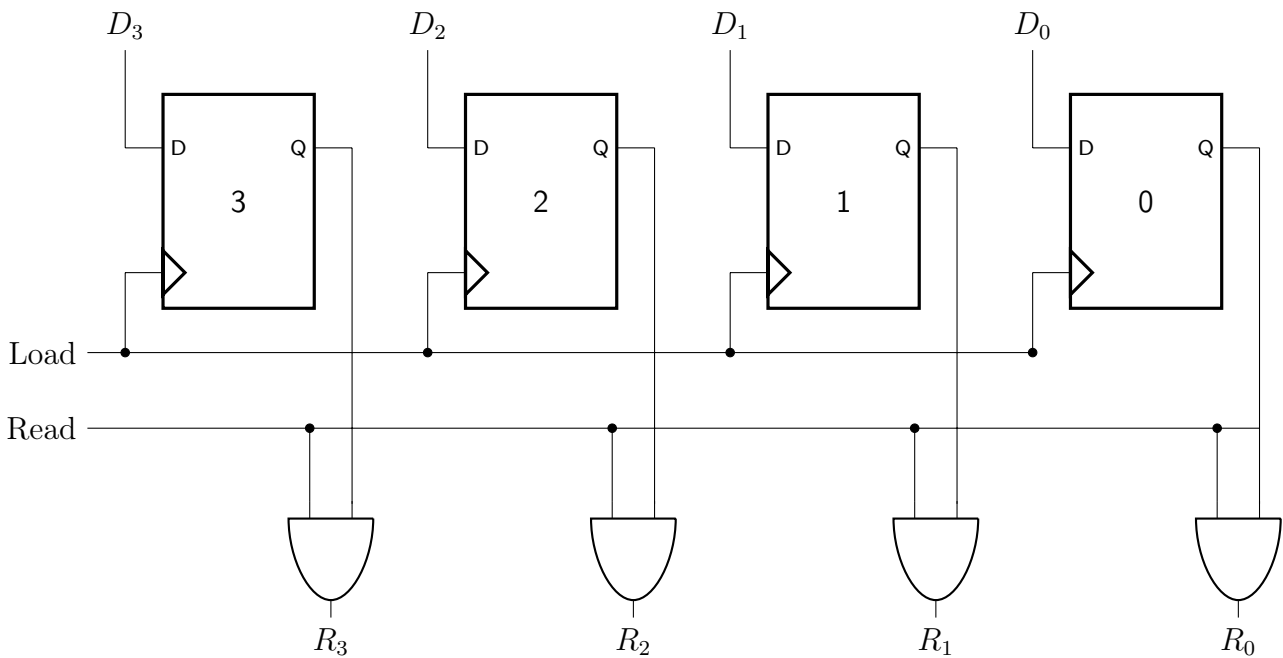


Figure 1: Logic circuit

Task 3

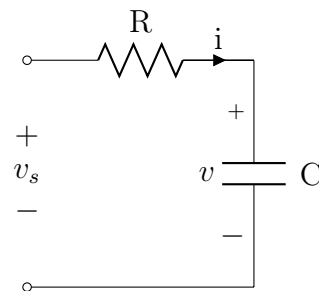


Figure 2: RC circuit

Kirchoff's Voltage Law of Figure 2 gives the differential equation

$$\tau \frac{dv}{dt} = -v + v_s$$

where $\tau = RC$.

Task 3.a

Show that

$$v(t) = V_0 e^{-\frac{t}{\tau}}$$

is a solution to the differential equation when $v_s = 0$ and $v(t = 0) = V_0$.

Make a sketch of $v(t)$, and calculate $v(t)$ for $t = \tau$, $t = 2\tau$ and $t = 5\tau$.

Task 3.b

Show that the tangent to $v(t)$ at $t = 0$ intersects the zero line at $t = \tau$.

Task 3.c

Show that

$$v(t) = V_s(1 - e^{-\frac{t}{\tau}})$$

is a solution when $v_s = V_s$ and $v(t = 0) = 0$.

Make a sketch of $v(t)$.

Task 3.d

Given $C = 1 \mu\text{F}$ and we want $\tau = 0.1 \text{ s}$. Find R .

If $v_s = 5 \text{ V}$, what is $v(t = \tau)$?

Task 3 Solution

Task 3.a Solution

When $v_s = 0$ we have the equation:

$$\frac{dv}{dt} = -\frac{1}{\tau}v$$

By using the exponential decay equation we get:

$$v(t) = v(0)e^{-\frac{t}{\tau}} = V_0e^{-\frac{t}{\tau}}$$

Calculating $t = \tau$:

$$v(t = \tau) = V_0e^{-1} = \frac{V_0}{e}$$

Calculating $t = 2\tau$:

$$v(t = \tau) = V_0e^{-2} = \frac{V_0}{e^2}$$

Calculating $t = 5\tau$:

$$v(t = \tau) = V_0e^{-5} = \frac{V_0}{e^5}$$

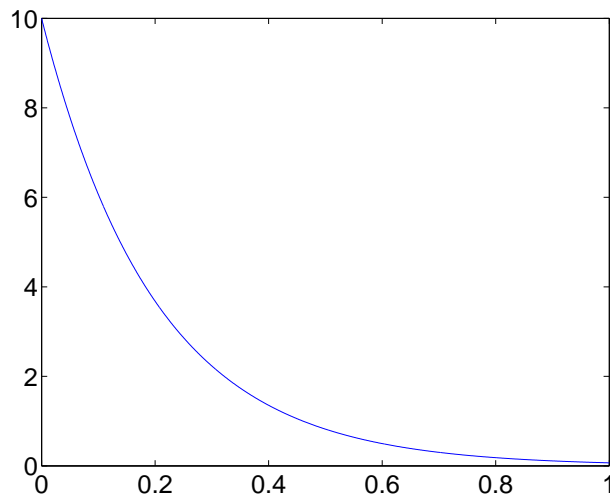


Figure 3: Plot of $v(t)$ with $V_0 = 10 \text{ V}$ and $\tau = \frac{1}{5}$

Task 3.b Solution

The tangent of $v(t = 0)$ is given as:

$$\begin{aligned} y - V_0 &= \frac{dv}{dt}(0) \cdot (t - 0) \\ y - V_0 &= -V_0 \frac{1}{\tau} t \\ y &= -V_0 \frac{1}{\tau} t + V_0 \end{aligned}$$

The zero line is when $y = 0$:

$$\begin{aligned} 0 &= -V_0 \frac{1}{\tau} t + V_0 \\ V_0 \frac{1}{\tau} t &= V_0 \\ t &= \tau \end{aligned}$$

Task 3.c Solution

$$\begin{aligned} \tau \frac{dv}{dt} &= -v + v_s \\ \Rightarrow \frac{dv}{dt} &= -\frac{1}{\tau} v + \frac{1}{\tau} v_s \end{aligned}$$

Solving the differential equation we get

$$v(t) = V_s(1 - e^{-\frac{t}{\tau}})$$

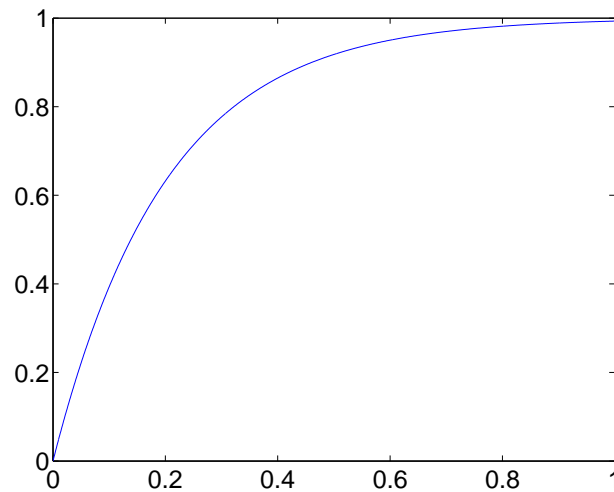


Figure 4: Plot of $v(t)$ with $V_s = 10$ V and $\tau = \frac{1}{5}$

Task 3.d Solution

$$\tau = RC \Rightarrow R = \frac{\tau}{C} = \frac{0.1}{10^{-1}} = \underline{\underline{100 \text{ k}\Omega}}$$

$$v(t) = V_s(1 - e^{-\frac{t}{\tau}})$$

$$v(t) = 5(1 - e^{-\frac{t}{\tau}})$$

$$\underline{\underline{v(t) = 5(1 - e^{-\frac{t}{\tau}})}}$$

Task 4

Task 4.a

Show by using a truth table that:

$$A + 1 = 1$$

$$A + 0 = A$$

$$A \cdot 1 = A$$

$$A \cdot 0 = 0$$

Task 4 Solution

Task 4.a

It can be seen in Table 1 that column 2 and 3 are equal.

It can be seen in Table 2 that column 1 and 3 are equal.

It can be seen in Table 3 that column 1 and 3 are equal.

It can be seen in Table 4 that column 2 and 3 are equal.

A	1	A + 1
0	1	1
1	1	1

Table 1: Truth table for $A + 1 = 1$

A	0	A + 0
0	0	0
1	0	1

Table 2: Truth table for $A + 0 = A$

Task 5

The pins 0 to 7 on the Arduino are mapped to a 1 byte register called PORTD. If bit $b_3 = 0$ in PORTD, then pin 3 will be 0 V, while if $b_3 = 1$, then pin 3 will be 5 V.

Task 5.a

Lets assume that the value of PORTD is $A7_{16}$. What are the voltages on pins 0-7?

Task 5.b

By using $\text{PORTD} = \text{PORTD} | x$, you can change a pin from 0 V to 5 V. For instance: $x = 8_{16}$ will change pin 4.

Which values of x will change pins 7 and 5 if $\text{PORTD} = A7_{16}$?

Task 5.c

By using $\text{PORTD} = \text{PORTD} \& !x$, you can change a pin from 5 V to 0 V. For instance: $x = 4_{16}$ will change pin 3.

Which values of x will change pins 8, 6 and 2 if $\text{PORTD} = A7_{16}$?

Task 5 Solution

Task 5.a

Pins 0, 1, 2, 5 and 7 are 5 V, while 3, 4 and 6 are 0 V.

Task 5.b

In order to change pin 7 we must have $x = 1 \ll 7 = 40_{16}$.

In order to change pin 5 we must have $x = 1 \ll 5 = 10_{16}$.

A	1	$A \cdot 1$
0	1	0
1	1	1

Table 3: Truth table for $A \cdot 1 = A$

A	0	$A \cdot 0$
0	0	0
1	0	0

Table 4: Truth table for $A \cdot 0 = 0$

Task 5.c

In order to change pin 8 we must have $x = 1 \ll 8 = 80_{16}$.

In order to change pin 6 we must have $x = 1 \ll 6 = 20_{16}$.

In order to change pin 2 we must have $x = 1 \ll 2 = 4_{16}$.